

2. ábra: A 8. feladat áramköre

$$A.) \quad Z_e = 20 - 20j + (20 \times 20j) =$$

$$= 20 - 20j + \frac{20 \cdot 20j}{20 + 20j} =$$

$$= 20 - 20j + 10 + 10j = \underline{\underline{30 - 10j}} \quad (1)$$

$$\hat{i} = \frac{U}{Z_e} = \frac{100}{30 - 10j} = \underline{\underline{3 + 1j}} \quad (1)$$

$$\hat{i}_L = \hat{i} \cdot \frac{20}{20 + 20j} = \underline{\underline{2 - 1j}} \quad (0.5)$$

$$i_e = \hat{i} - \hat{i}_L = 3 + 1j - (2 - 1j) = \underline{\underline{1 + 2j}} \quad (0.5)$$

if w (omega) gets halved Zc gets doubled

$$B.) \quad Z'_c \Rightarrow Z'_c = \frac{1}{j\omega C}$$

w felére csökken: Zc duplájára nő

$$Z'_c = -40j$$


if w (omega) gets halved ZL gets halved as well

$$Z'_L = j\omega L$$

w felére csökken: ZL felére csökken


$$Z'_e = 20 + (-40j) + (20 \times 10j) = 20 - 40j + \frac{20 \cdot 10j}{20 + 10j} =$$

$$= 20 - 40j + 4 + 8j = \underline{\underline{24 - 32j}} \quad (1)$$

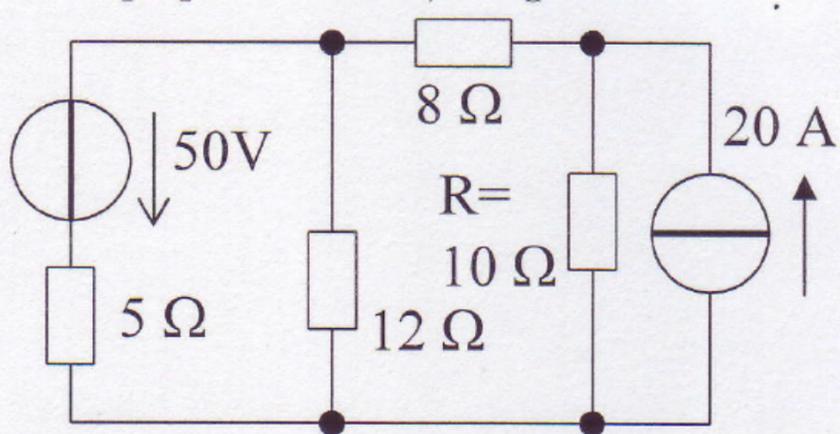

3. ábra: A 9. feladat áramköre

Superpozíció 1. eset

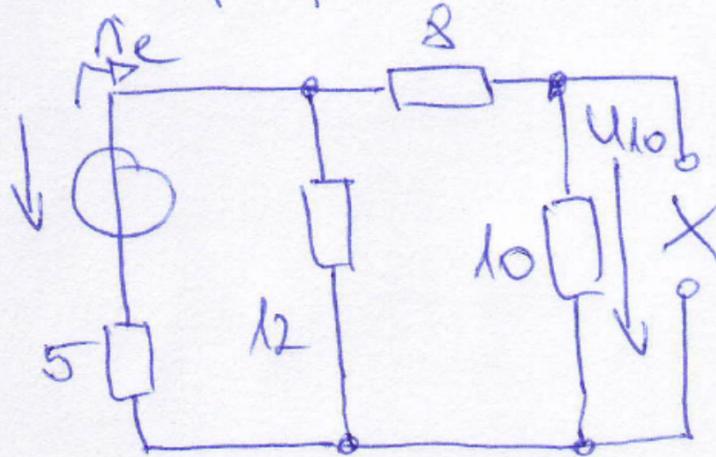



$$U_{10} = ?$$

$$R_e = 5 + 12 \times (8 + 10) = 12,2 \Omega$$

$$I_{10} = I_e \cdot \frac{12}{12 + (10 + 8)} = 4,1 \cdot \frac{12}{30} = 1,64 \text{ A}$$

$$U_{10} = 10 \cdot 1,64 \text{ A} = 16,4 \text{ V} \downarrow \quad (1,5)$$

Superpozíció 2. eset

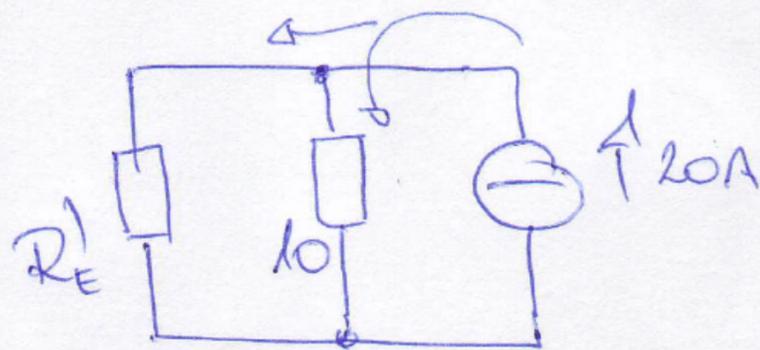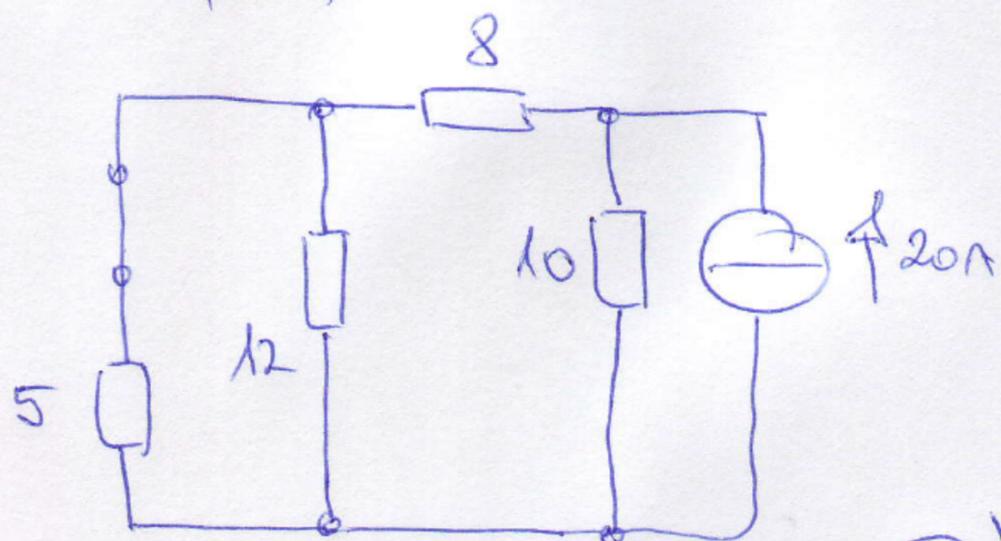

$$R'_E = (5 \times 12) + 8 = 11,53 \Omega$$

$$I_{10} = 20 \text{ A} \cdot \frac{11,53}{11,53 + 10} = 10,71 \text{ A} \downarrow \quad U_{10} = 10 \cdot 10,71 = 107,1 \text{ V} \quad (1,5)$$


Superpozíció összegzés:

$$U_{10} = \sum U_{10_i} = 16,4 \text{ V} + 107,1 \text{ V} = \underline{\underline{123,5 \text{ V}}}$$

$$I_{10} = \frac{U_{10}}{10} = \underline{\underline{12,35 \text{ A}}}$$


$$P_{10} = U_{10} \cdot I_{10} = \underline{\underline{1525,2 \text{ W}}}$$

(1)

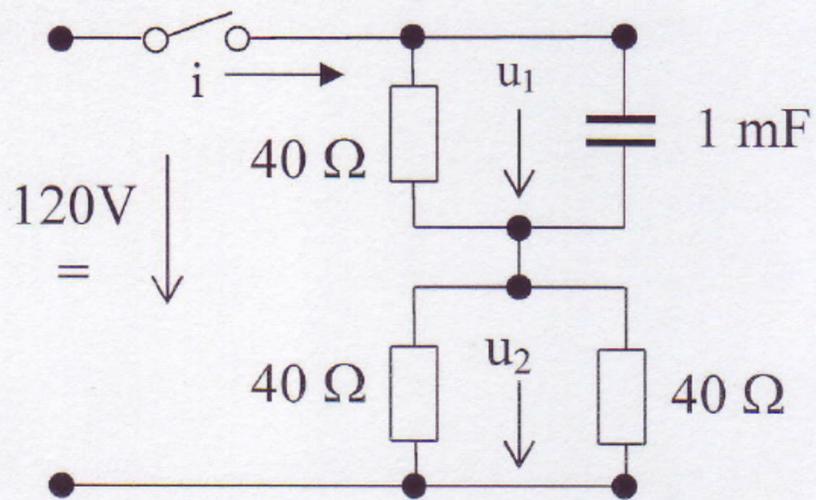

4. ábra: A 10. feladat áramköre

$t = 0$: C rövidzár
Short circuit

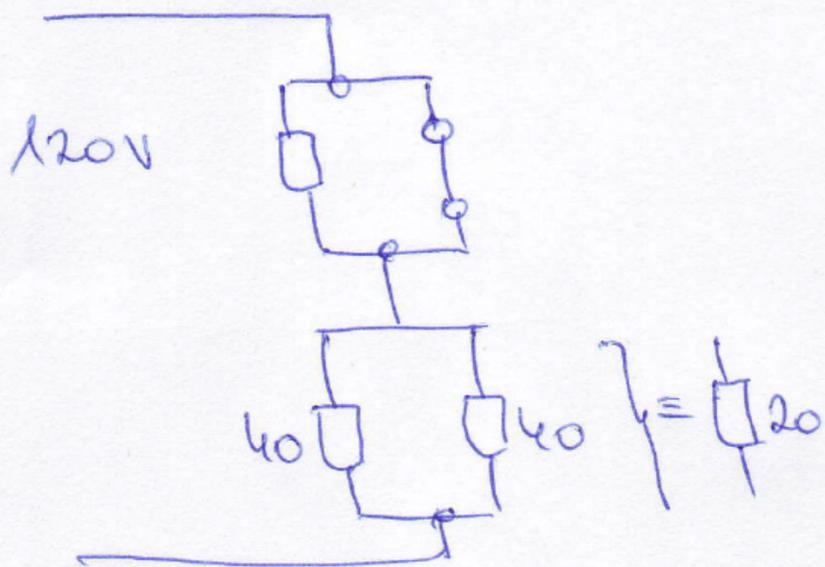


$U_1 = 0$ (C rövidzár)

$U_2 = 120V$

$i = \frac{120}{20} = 6A$

1

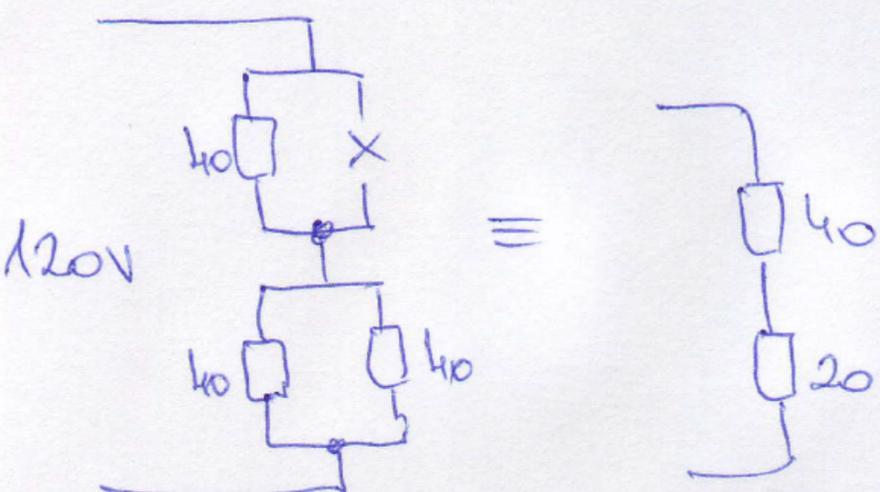$t \rightarrow \infty$: C szakadás
Open circuit




$U_1 = 120 \cdot \frac{40}{40+20} = 80V$

$U_2 = 120 \cdot \frac{20}{40+20} = 40V$

$i = \frac{120}{40+20} = 2A$

1

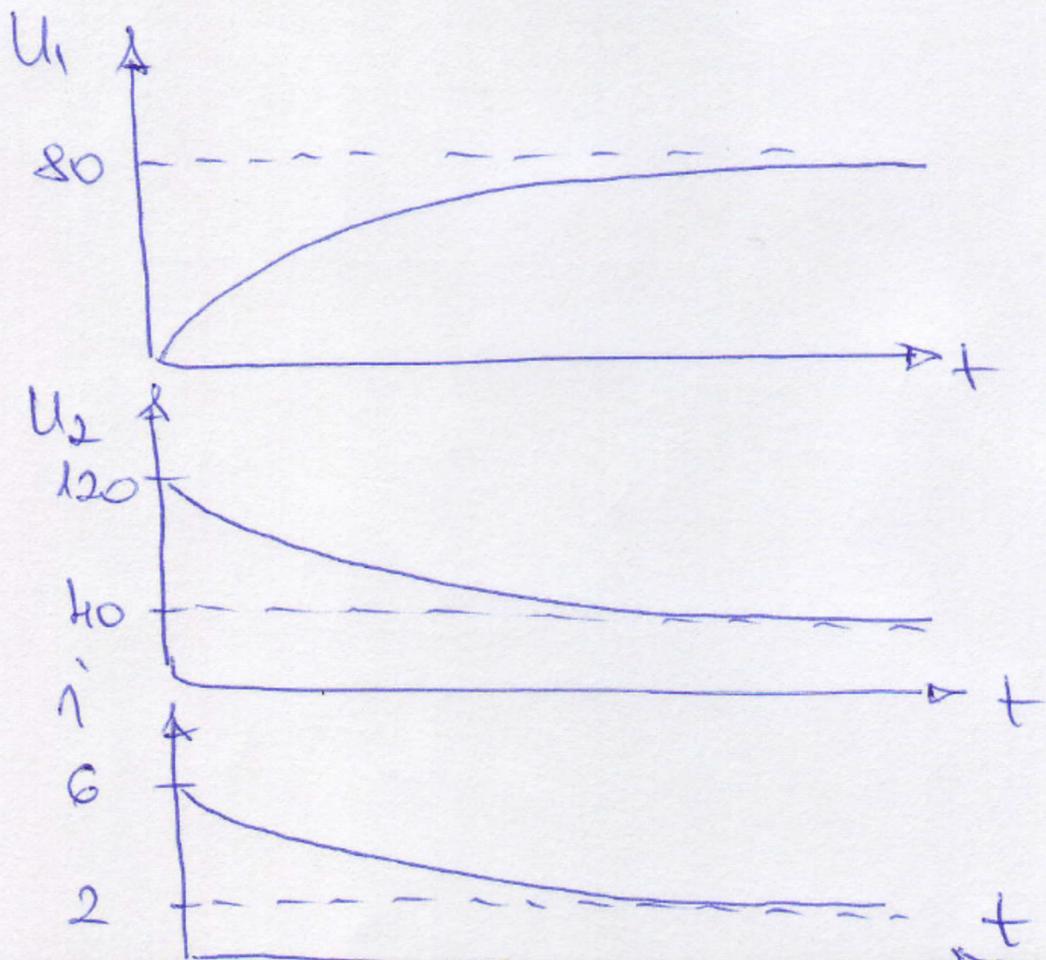

$U_1 = 80(1 - e^{-\frac{t}{T}})$


$U_2 = 40 + 80 \cdot e^{-\frac{t}{T}}$

$i = 2 + 4 \cdot e^{-\frac{t}{T}}$

1

$T = R^* \cdot C$


R^* :

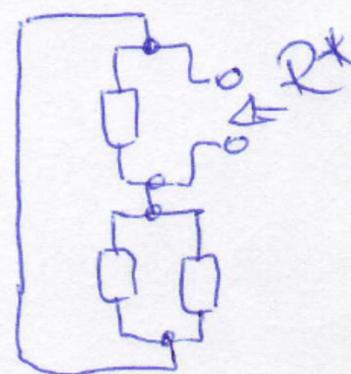

$R^* = 20 \times 40 \times 40 = 13,3 \Omega$

$T = 13,3 \mu s$

1

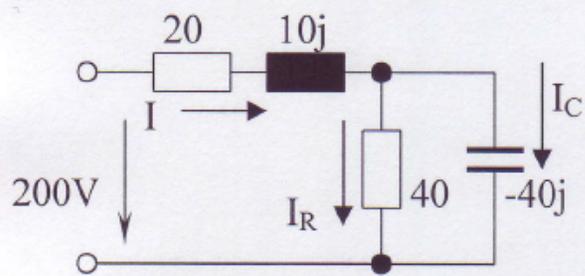

3. ábra: A 9. feladat áramköre

$$Z_e = 20 + 10j + (40 \times (-40j)) =$$

$$= 20 + 10j + 20 - 20j = \underline{\underline{40 - 10j}} \quad (17)$$

$$I = \frac{200}{40 - 10j} = \underline{\underline{4,7 + 1,17j}} \text{ (A)} \quad (0,5)$$

$$\hat{I}_C = I \cdot \frac{40}{40 - 40j} = (4,7 + 1,17j) \frac{40}{40 - 40j} = \underline{\underline{1,76 + 2,93j}} \text{ (A)} \quad (0,5)$$


$$\hat{I}_R = \hat{I} - \hat{I}_C = 4,7 + 1,17j - (1,76 + 2,93j) = \underline{\underline{2,94 - 1,76j}} \text{ (A)} \quad (0,5)$$

Fele frekvencián: On half w (omega)

$$10j \Rightarrow 5j \quad -40j \Rightarrow -80j$$

$$Z_e = 20 + 5j + (40 \times (-80j)) =$$

$$= 20 + 5j + 32 - 16j = \underline{\underline{52 - 11j}} \quad (1,5)$$

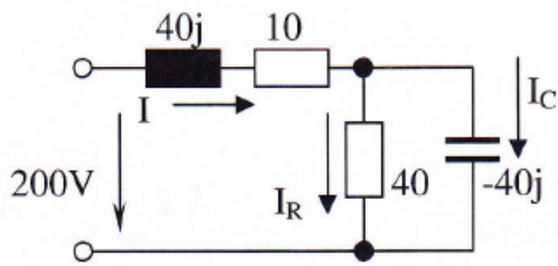


3. ábra: A 9. feladat áramköre


$$\begin{aligned}
 Z_c &= 40j + 10 + (40 \times -40j) = \\
 &= 40j + 10 + \frac{-1600j}{40 - 40j} = \quad (1) \\
 &= 40j + 10 + 20 - 20j = 30 + 20j \text{ (}\Omega\text{)}
 \end{aligned}$$

$$\begin{aligned}
 I &= I_L = I_{Rc} = \frac{200}{30 + 20j} = \frac{60 - 40j}{13} = 4,61 - j3 \text{ (A)} \\
 I_c &= I \cdot \frac{40}{40 - 40j} = (4,61 - j3) \cdot \frac{4}{4 - 4j} = (4,61 - j3)(0,5 + j0,5) = \\
 &= 3,8 + j0,8 \text{ (A)} \\
 I_R &= I - I_c = (4,61 - j3) - (3,8 + j0,8) = 0,81 - j3,8 \text{ (A)}
 \end{aligned}$$

$$\begin{aligned}
 U_L &= I \cdot 40j = (4,61 - j3) 40j = 120 + j184,4 \text{ (V)} \\
 U_R &= I \cdot 10 = 46,1 - j30 \text{ (V)} \\
 U_{Rc} &= U - U_L - U_R = 33,9 - j\frac{154,4}{1} \text{ (V)}
 \end{aligned}$$

Phasor diagram

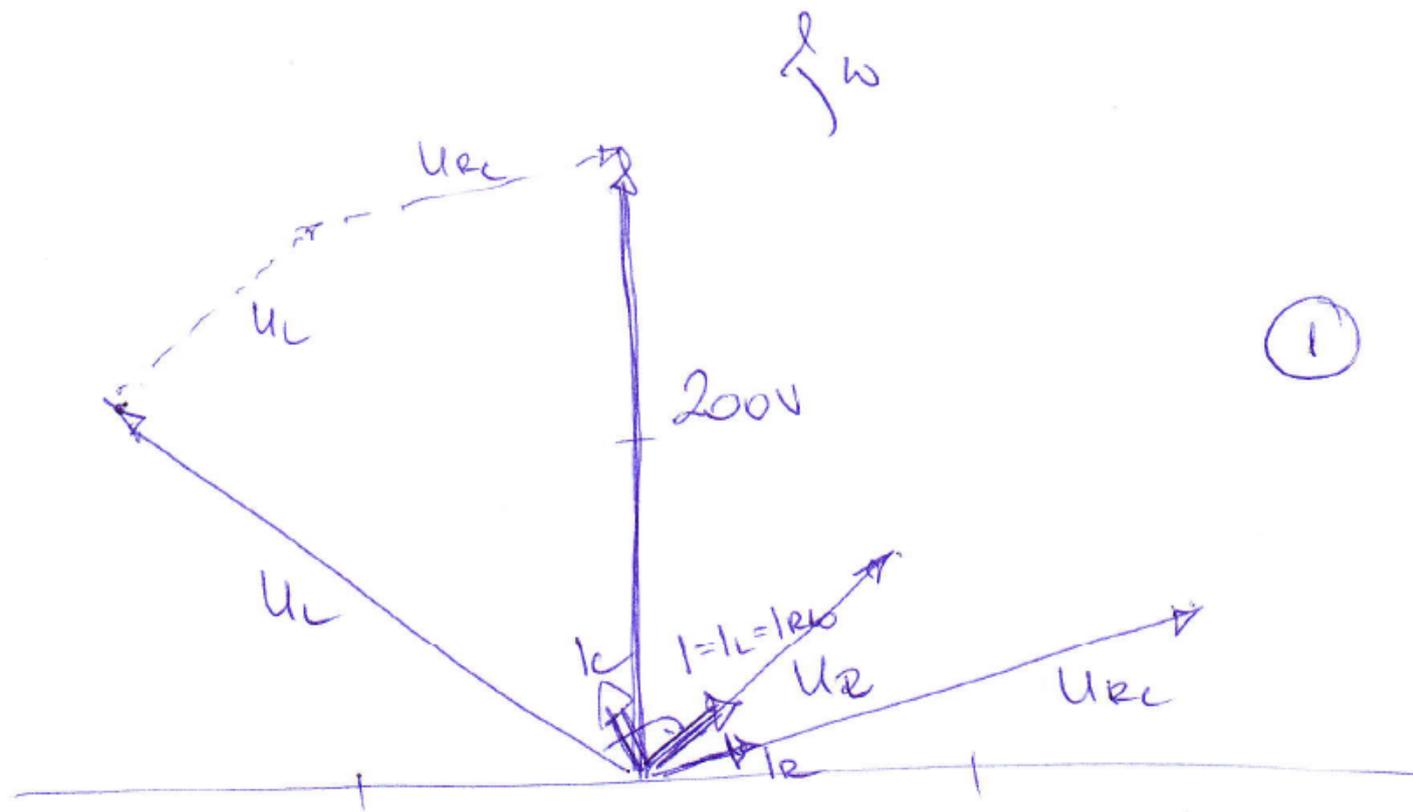

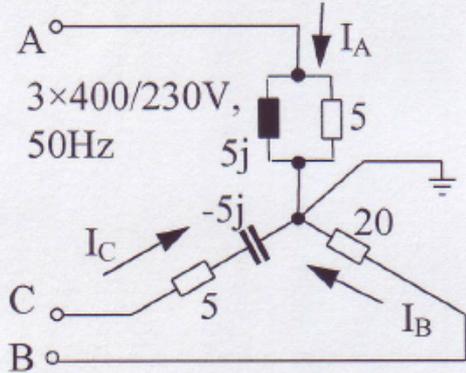

2. ábra: A 8. feladat áramköre

$$a.) \quad \dot{I}_A = \frac{230}{5j} + \frac{230}{5} = 46 - j46 \text{ A}$$

$$|\dot{I}_A| = \sqrt{46^2 + 46^2} = 65 \text{ A}$$

$$\dot{I}_B = \frac{230}{20} = 11,5 \text{ A}$$


$$|\dot{I}_B| = 11,5 \text{ A}$$

$$\dot{I}_C = \frac{230}{5-5j} = \frac{230}{5-5j} \cdot \frac{5+5j}{5+5j} = \frac{230 \cdot 5 + 230 \cdot 5j}{50} = 23 + 23j \text{ A}$$

$$|\dot{I}_C| = \sqrt{23^2 + 23^2} = 32,52 \text{ A}$$

(1)

b.)

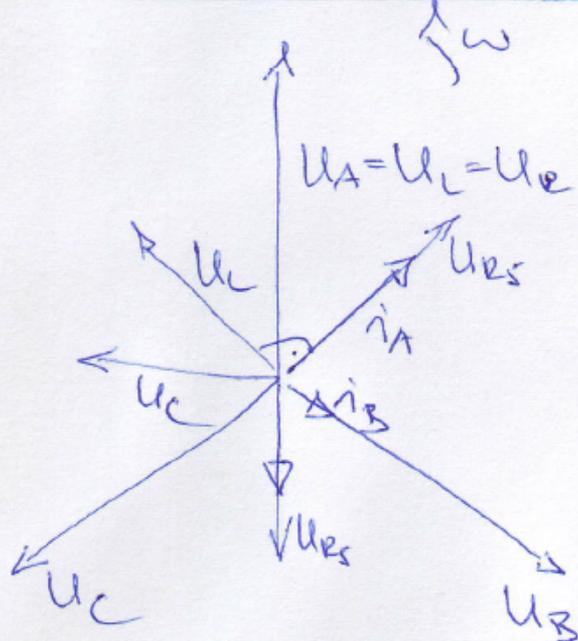

(1)

c.) $\hat{I}_C = \phi$ $\hat{I}_A = \hat{I}_B$ A_2 A-B ág vonali

fémültnégre kerül.


If we disconnect C phase, V_{AB} will be the line to line voltage

(1)

$$Z = (5 \times 5j) + 20 = 22,5 + 25j$$

$$\hat{I}_A = \hat{I}_B = \frac{400}{22,5 + 25j} = 11,75 - 0,19j \text{ A}$$

$$|\hat{I}_A| = \sqrt{11,75^2 + 0,19^2} = 11,76$$

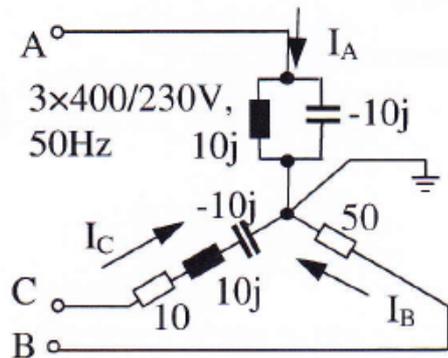


2. ábra: A 8. feladat áramköre

$$I_A = \frac{230}{10j \times (-10j)} = \phi \quad |I_A| = \phi$$

$$I_B = \frac{230}{50} = 4,6 \text{ A} \quad |I_B| = 4,6 \text{ A}$$

$$I_C = \frac{230}{10 + 10j - 10j} = 23 \text{ A} \quad |I_C| = 23 \text{ A} \quad (17)$$

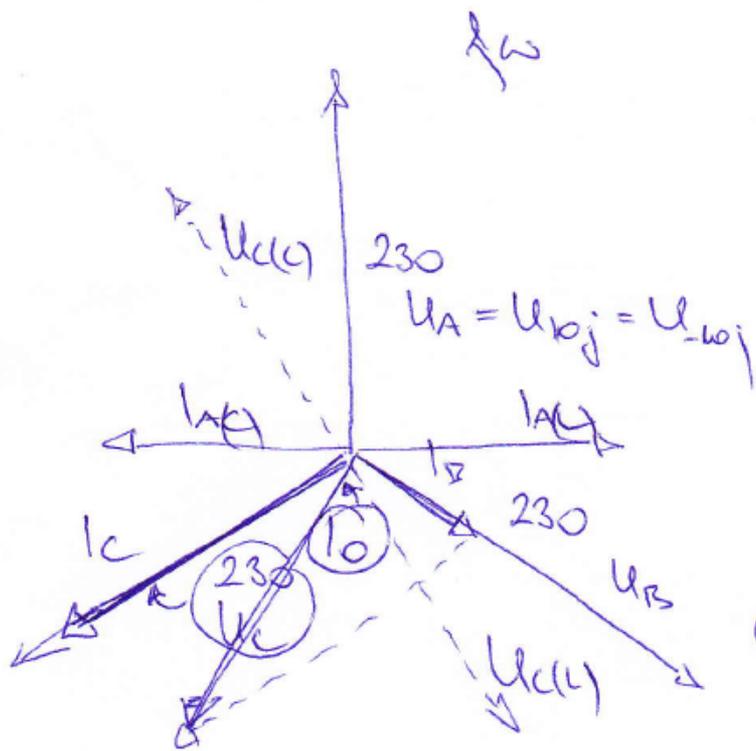

$$I_{A(L)} = \frac{230}{10j} = -23j \text{ A}$$

$$I_{A(C)} = \frac{230}{-10j} = 23j \text{ A} \quad (17)$$

$$U_{C(L)} = 23 \text{ A} \cdot 10j = 230j \text{ V}$$

$$U_{C(C)} = 23 \text{ A} \cdot (-10j) = -230j \text{ V}$$

(18)